


Raspberry Pi based Data-logger

SUPERVISOR: Professor Giacinta Parish
Student Name: ZHU QIAN
Student number: 22113255

9 Oct 2019

Introduction

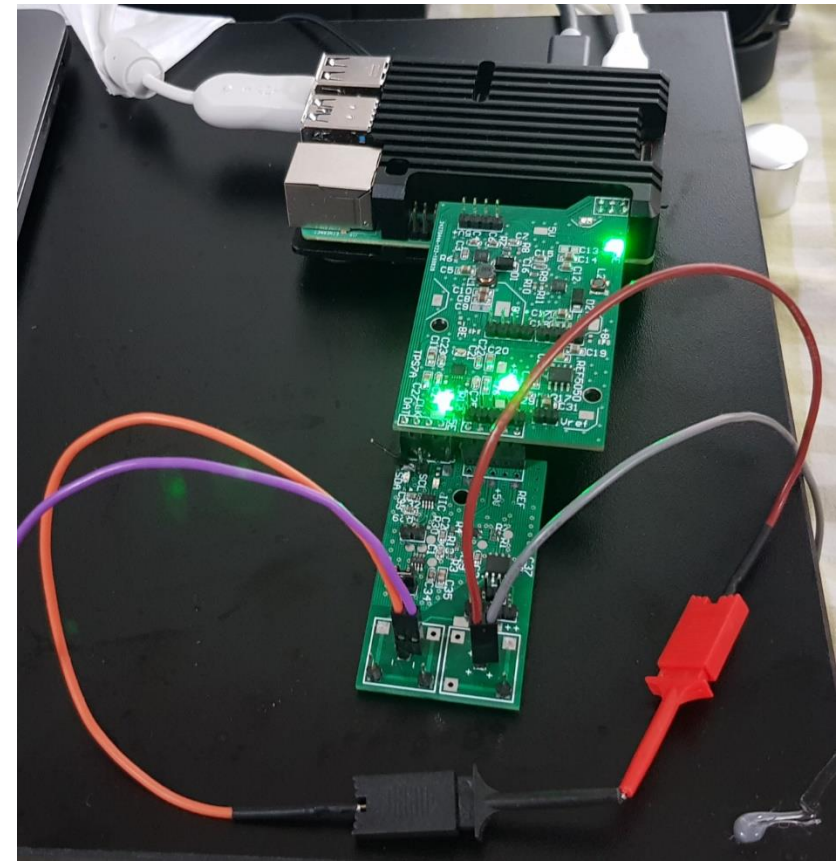1. Requirement
2. Hardware design
 - Power
 - Analog to Digital converter
3. Software design
 - Basic function
 - Human interface
4. Result
5. Conclusion




Raspberry Pi based Data-Logger


Requirements – Part1

Equipment using right now

Datalogger	NI 9239
USB Chassis	NI cDAQ -9171
Computer	Windows computer
Price>5000\$	Include software and hardware


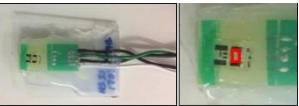


AlGaIn/GaN Sensor Device2 and Gate area

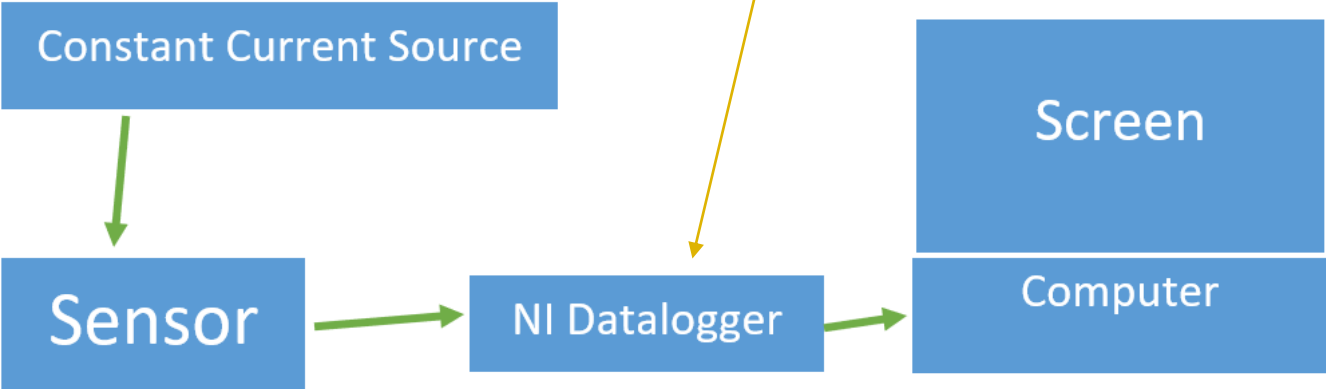

Requirements – Part2

Requirement	
Speed	>1kS/s
Input Range	$\pm 5V_{pp}$
Power supply	Directly powered by Raspberry Pi
Resolution	0.1mv

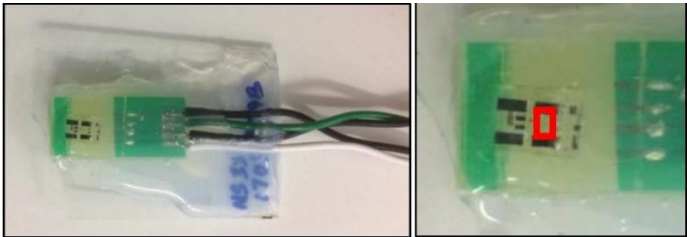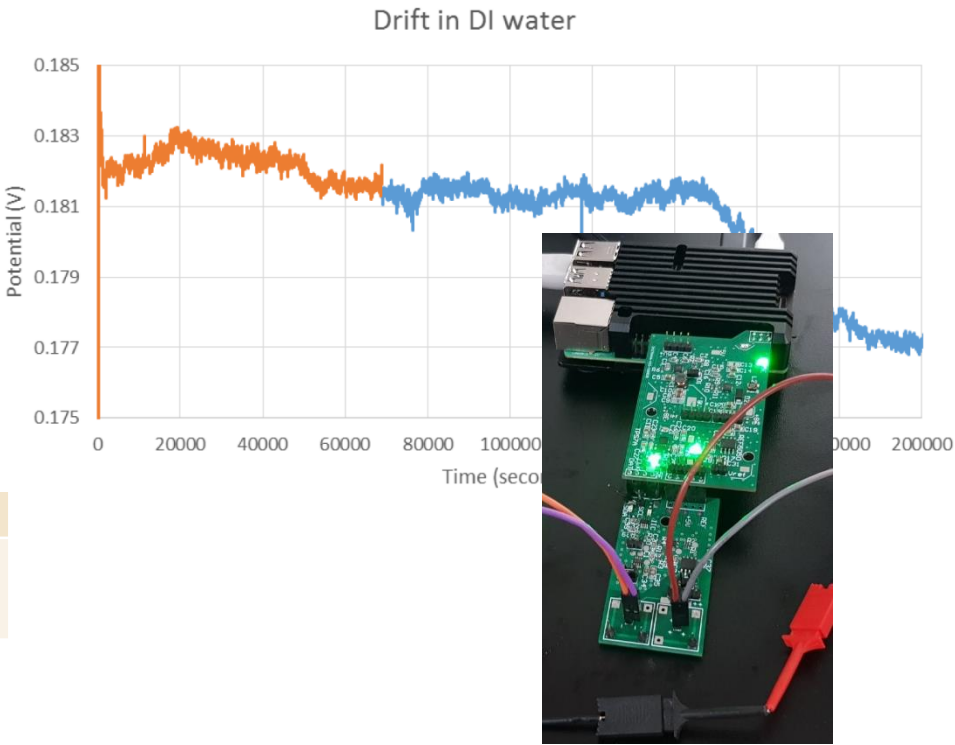

AlGaIn/GaN Sensor Device2
and Gate area (<10*10mm)

Constant Current Source


Sensor

Screen

Raspberry Pi

Hardware

Hardware Design – Power supply Part1

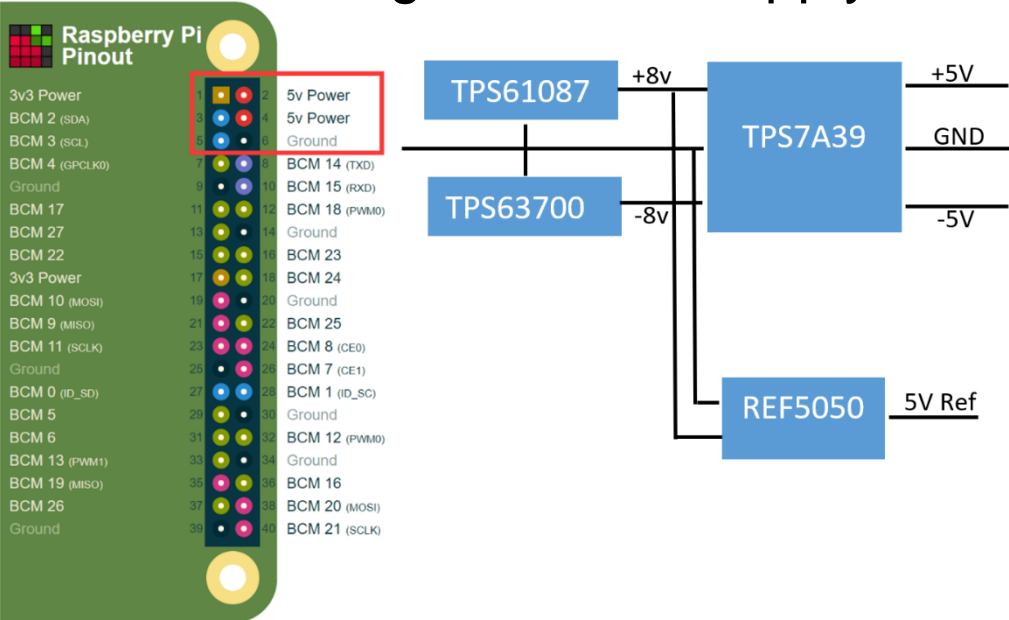


TPS61087 and TPS63700


- Buck and boost converter switch at 1.2MHz
- 10-Pin QFN Package

TPS7A39

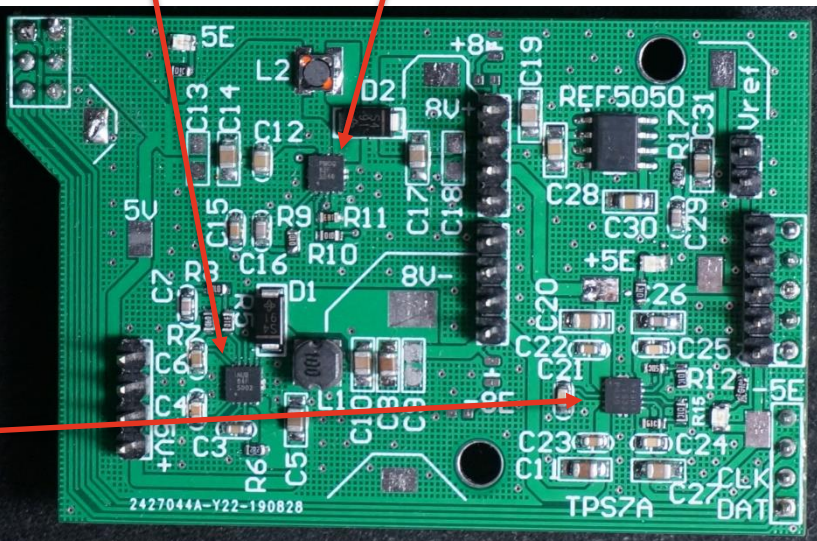- High-Precision Positive and Negative LDOs for High-Precision Analog Circuitry.
- High Power-Supply Rejection Ratio 69dB(120Hz) and >50dB(10Hz to 2Mhz)
- 150mA per Channel




Hardware Design – Power supply Part2

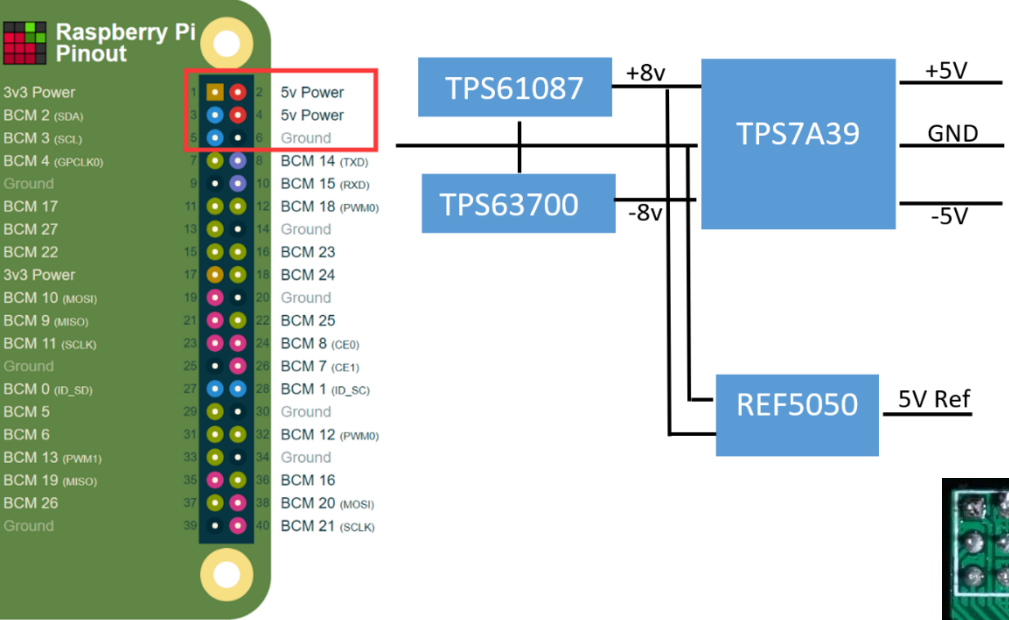



REF5050

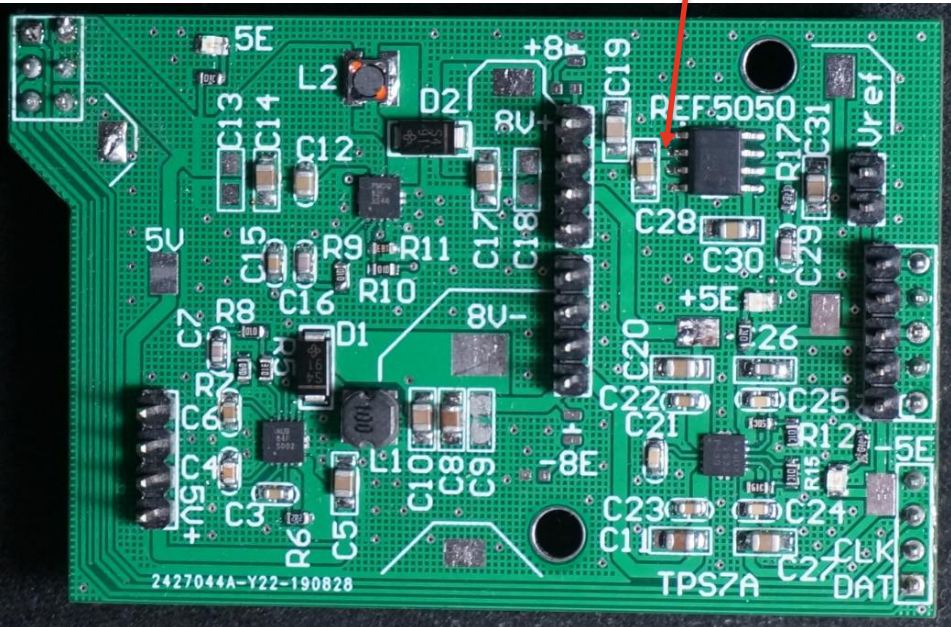- Low temperature Drift:
-Standard-Grade:8ppm/°C (Max)
- High Accuracy
-Standard-Grade:0.1%(MAX)
- Low Noise: 3 μ Vpp/V
- Excellent Long-Term Stability




Raspberry Pi based Data-Logger

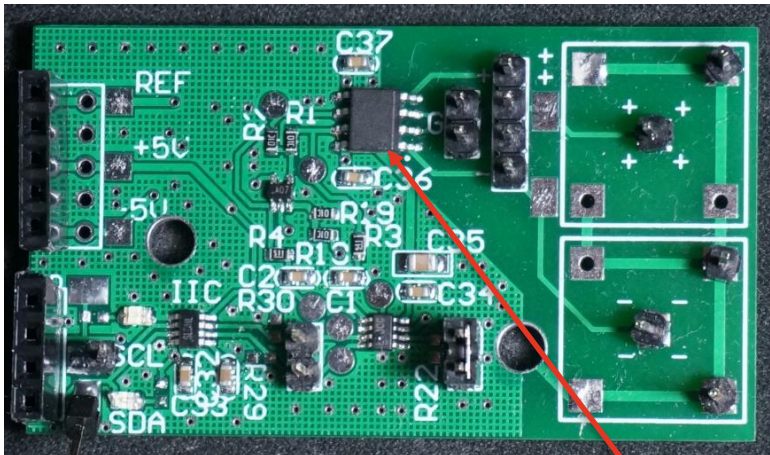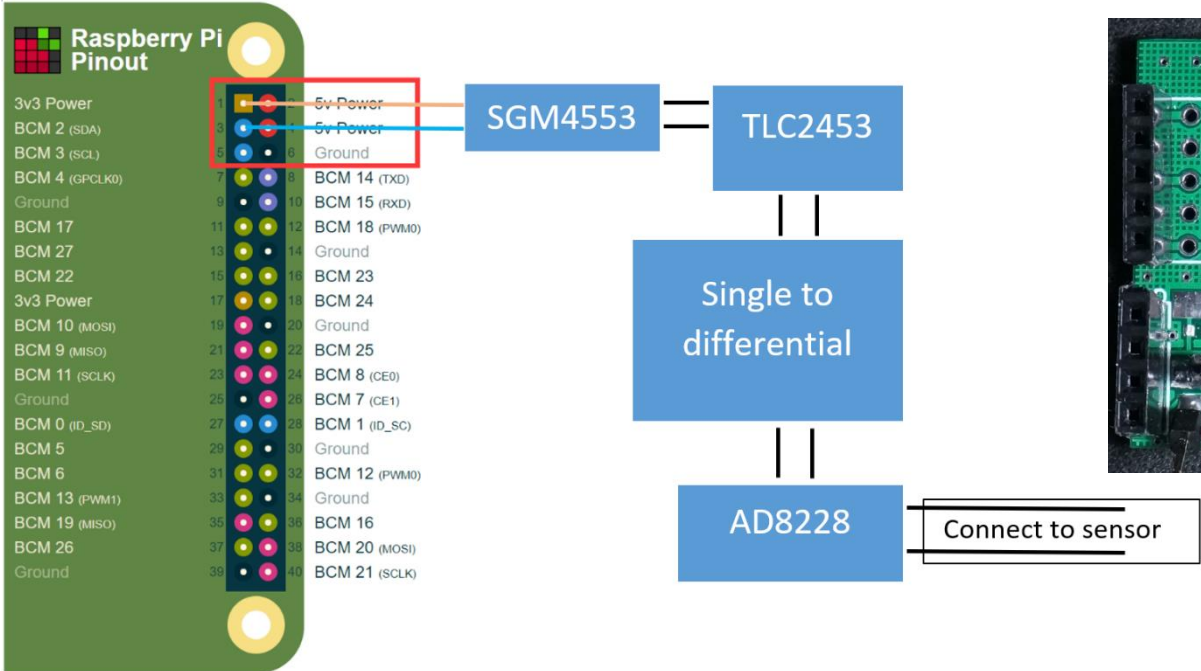Hardware Design – ADC converter and front end Part1



CONNECTION DIAGRAM

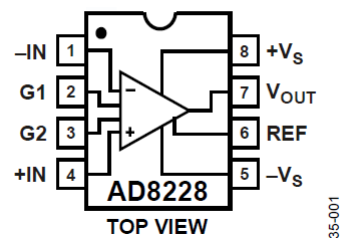


AD8228

- High performance instrumentation amplifier with very high gain accuracy.
- Pin strappable gains of 10 and 100.
- Low noise: 8 nV/ $\sqrt{\text{Hz}}$ 0.3uVpp from 0.1Hz to 10Hz

Raspberry Pi based Data-Logger

Hardware Design – ADC converter and front end Part2



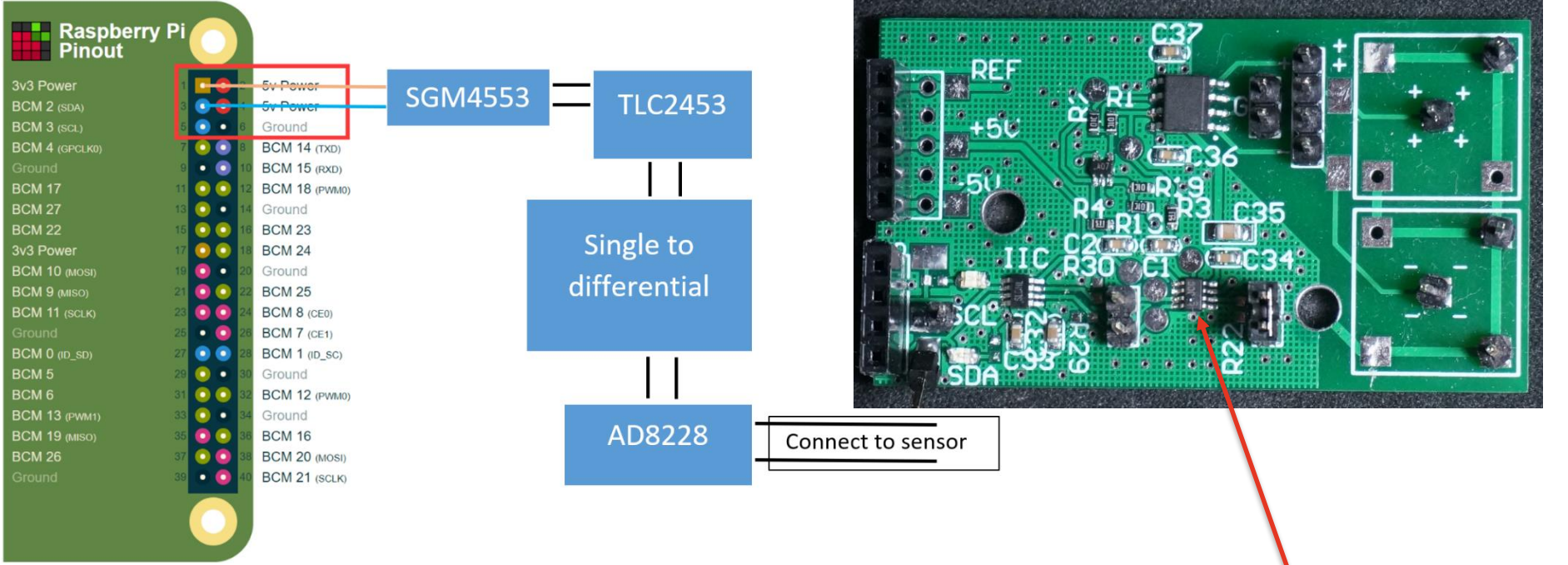


LTC2453

- 16Bit $\Delta\Sigma$ ADC with I2C interface
- 2LSB offset Error
- Differential input range
- 60 conversions Per Second


Raspberry Pi based Data-Logger

Hardware Design – Result

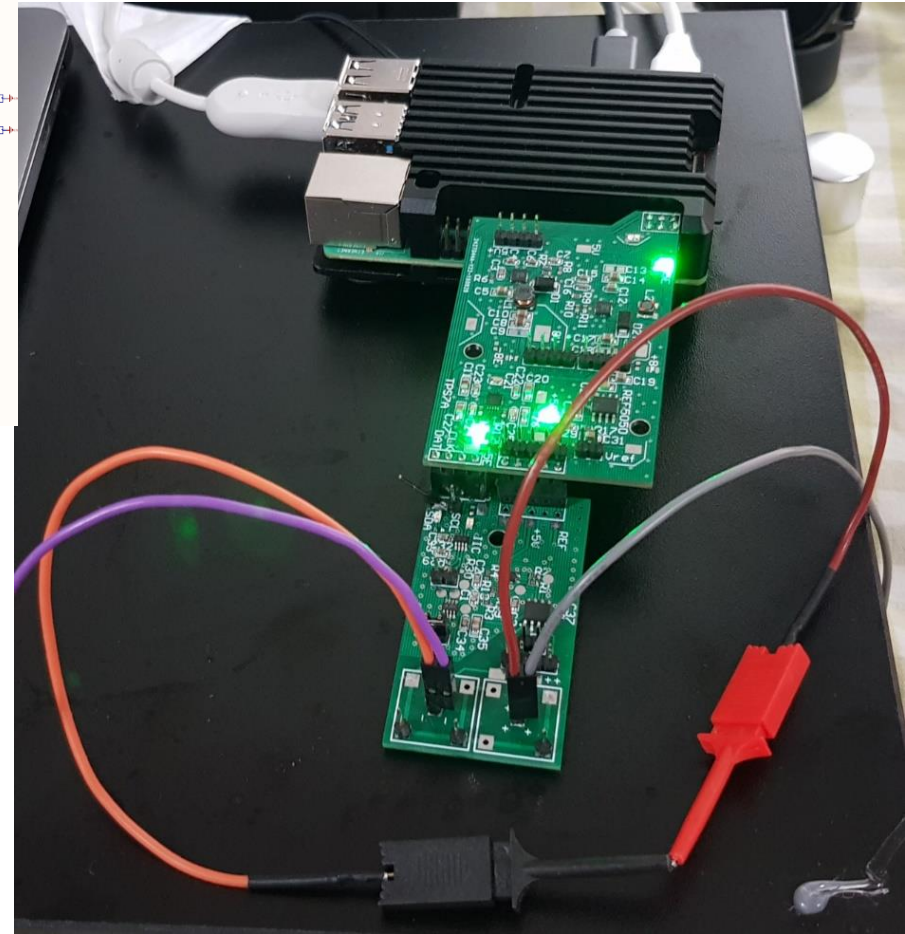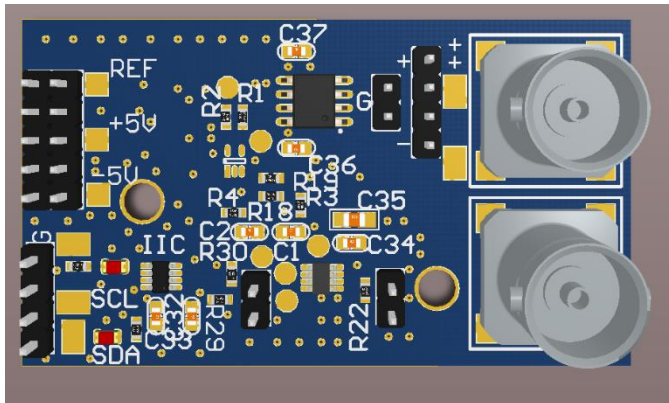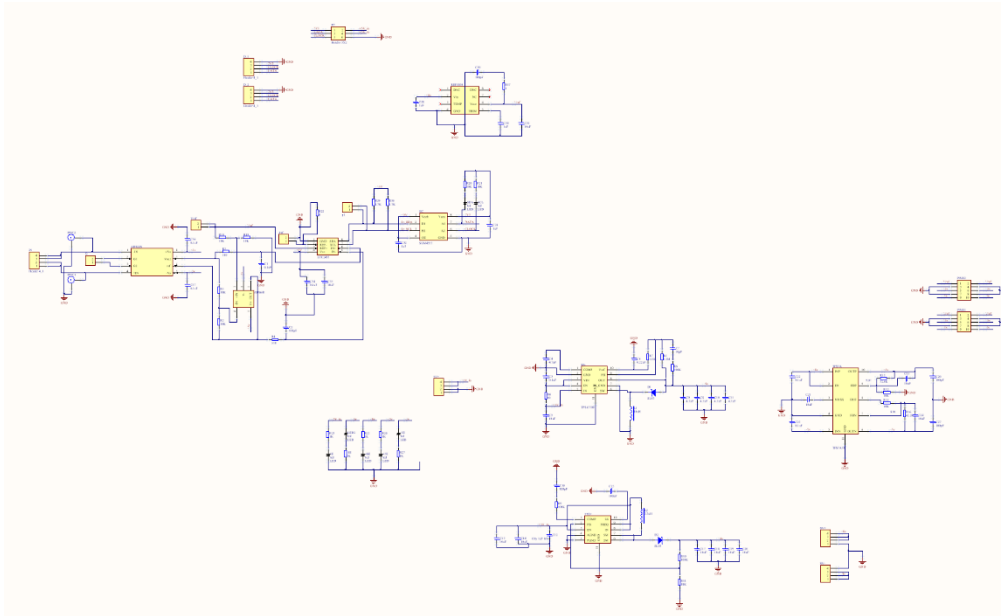

Raspberry Pi based Data-Logger


Hardware Design – Result

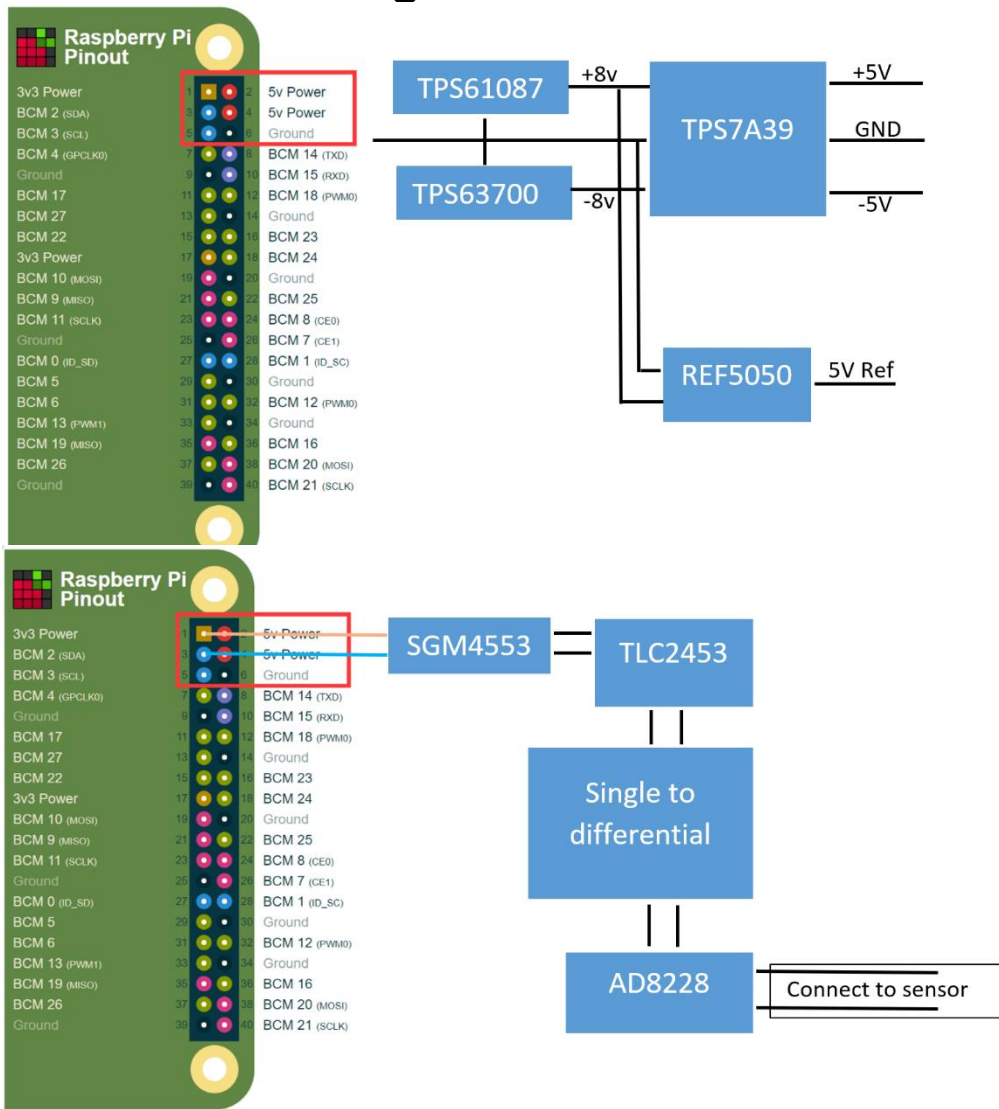

Raspberry Pi based Data-Logger

Software Design

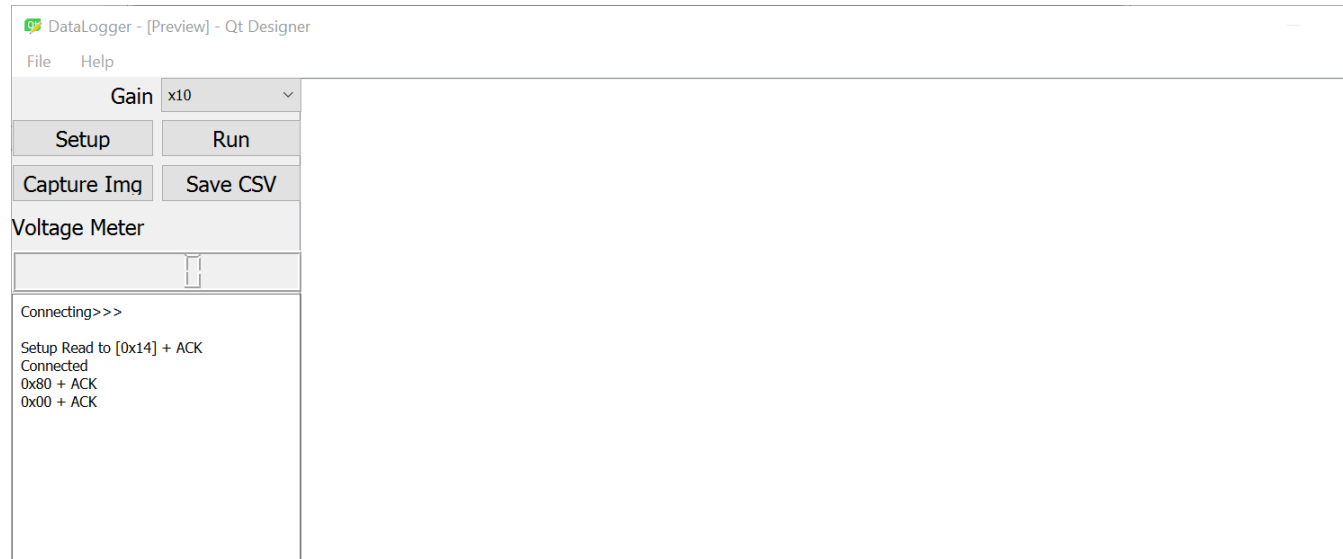- Smbus2
 - I2C interface to let Raspberry pi can easy to communicate with ADC
- QT PySide2 for Raspberry Pi
 - A official Python module from Qt for Python project. Which provide access to the complete Qt 5.12+ framework.
- Matplotlib for 2D plotting
 - A Python 2D plotting library which publication quality figures in Python scripts




Raspberry Pi based Data-Logger



Software Design – I2C interface

- smbus2_0.30
Pure Python
Drop-in replacement of smbus
easy to use directly in Python


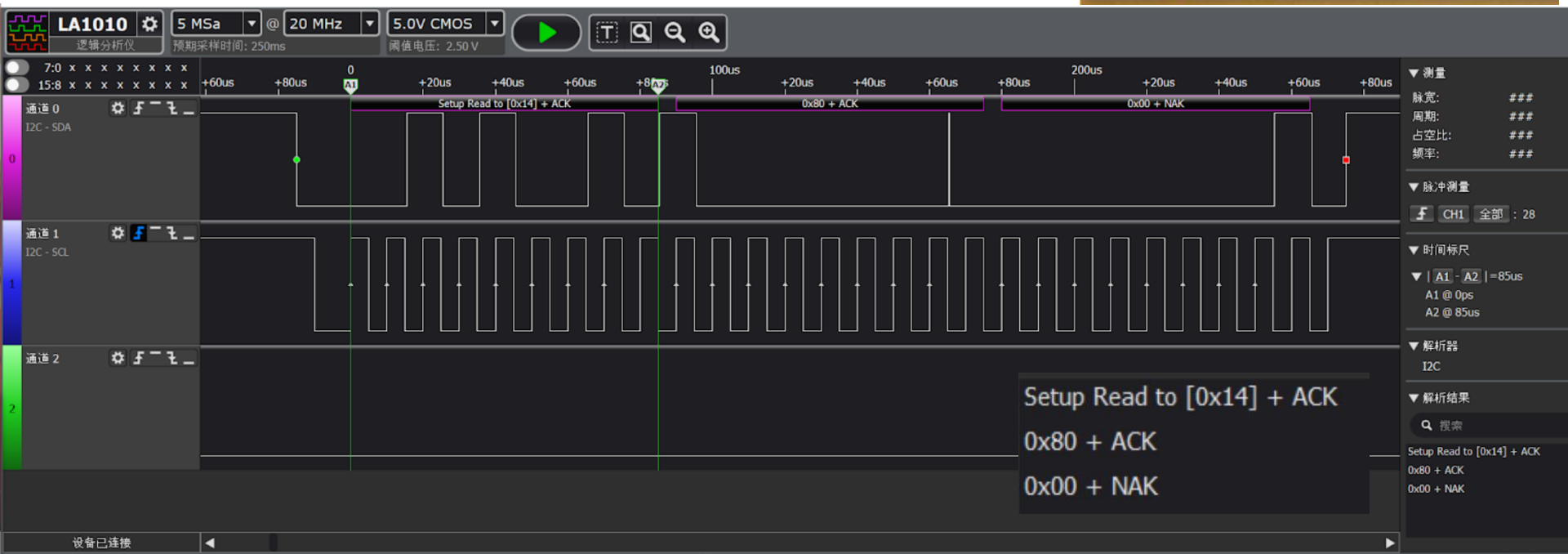
```
>>> b = bus.i2c_rdwr(msg)
>>> data = list(msg)
>>> print(len(data))
2
>>> print(data)
[128, 0]
>>> 
```



Raspberry Pi based Data-Logger

Software Design – PySide2

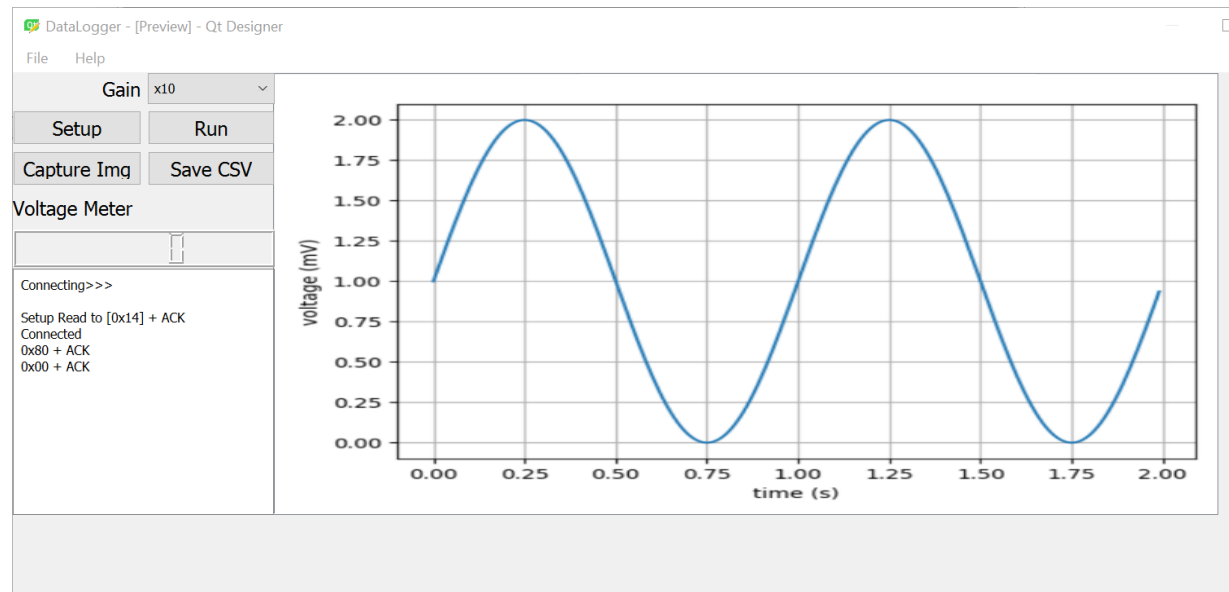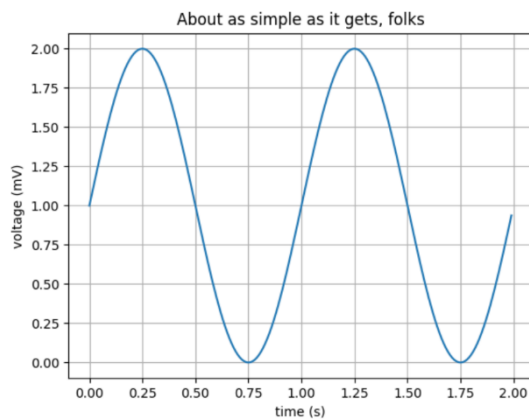- QT PySide2 for Raspberry Pi
A official Python module from Qt for Python project. Which provide access to the complete Qt 5.12+ framework.
- Matplotlib for 2D plotting
A Python 2D plotting library which publication quality figures in Python scripts




Raspberry Pi based Data-Logger

Result

- Price


		Prices(\$)
Single Board Computer	Raspberry Pi4 2G RAM	60
Analog to Digital Converter	LT2453 16Bit	4.87
AMP	AD8228	7.9
Voltage reference	REF5050	4
DCDC Boost	TPS63700	2
DCDC Boost	TPS61087	2
High precise linear regulator	TPS7A39	6
PCB	5pcs PCB	3
Total		89.77

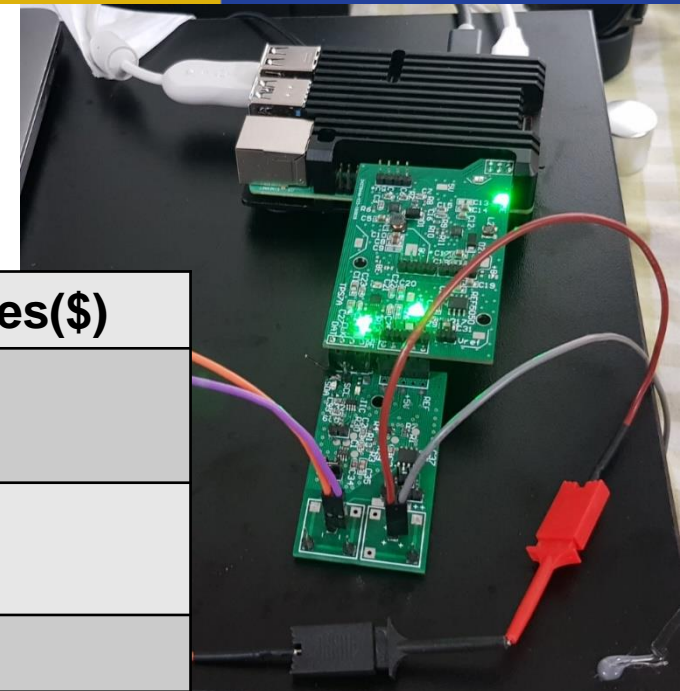

Raspberry Pi based Data-Logger

Conclusion

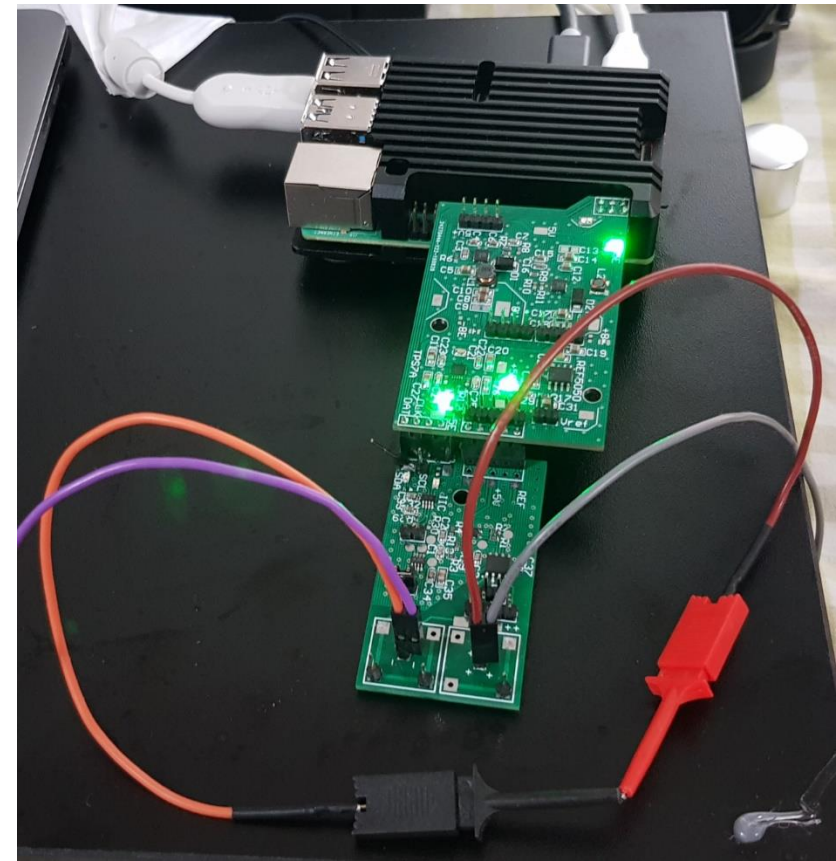- Future work
- Protection
- Isolate power supply



Thank you for listening

Also thanks for Brett, Gilberto and
Jeremy helps me a lot of this project